

#TapeThreading Kit



Join the dots with a bright light. These are easy to make with a bit of fine work, such as threading and taping. Decorating is adaptable.

The kit includes LED light with long wires, conductive tape, acrylic sheet with holes, a 3V button cell battery and a TronicBit battery holder.

For more information and video tutorial, go to monash.edu/it/making-for-all.

1. Thread LED wires through holes on both sides of sheet.
2. On back of sheet, use silver conductive tape to connect battery holder to wires. Red wire to positive side. Black wire to negative side. Make sure silver conductive tape only touches metal pads of battery holder.
3. On front of sheet, decorate with kit's and other materials.
4. Insert battery into holder with positive (+) side facing out.
5. Switch on.



WARNING

CHOKING HAZARD – Small part, button cell battery and sharp objects. Not for children under 3 years or any individuals who have a tendency to put inedible objects in their mouths.